

2021

ELECTRONICS — GENERAL

First Paper

Full Marks : 100

*The figures in the margin indicate full marks.**Candidates are required to give their answers in their own words as far as practicable.*



Group - A

Answer **question no. 1** and **any four** from the rest, taking **two** from each of **Unit-I** and **Unit-II**.1. Answer **any five** questions :

2×5

- State Kirchoff's current law.
- Define mutual inductance.
- Define one Farad of capacitance.
- State Norton's theorem.
- Write down the expression for the energy stored in an inductor.
- Define resistivity of a conductor.
- Draw the equivalent circuit of a practical voltage source.
- State Maximum Power Transfer theorem.


Unit - I

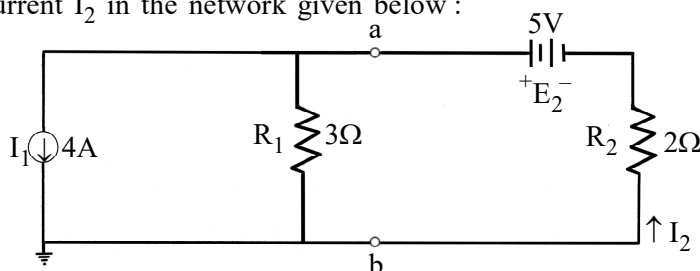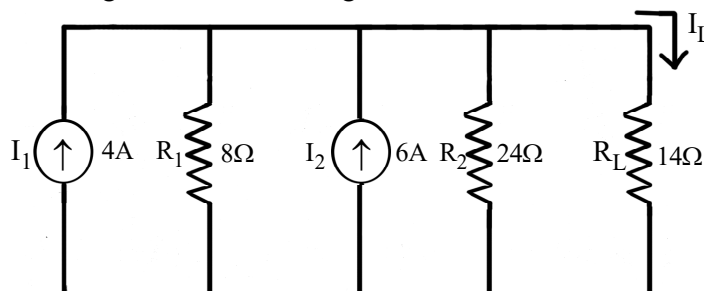2. (a) Determine current I_2 in the network given below :(b) Reduce the network given below to a single current source and calculate the current (I_L) through R_L .

5+5

Please Turn Over

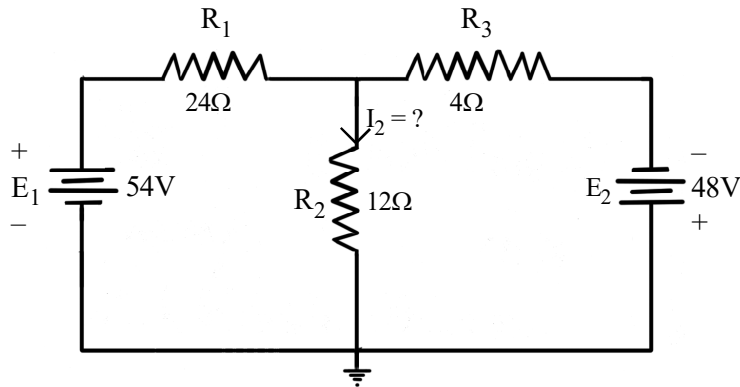3. (a) State Superposition theorem.
 (b) Using Superposition theorem, determine the current through the $12\ \Omega$ resistor in the figure given below.



- (c) What are active circuit elements? 2+6+2
4. (a) What do you mean by 'transient response' and 'steady state response' of a circuit?
 (b) A capacitor of capacitance C is fully charged with a battery of emf V_0 and is allowed to discharge through a resistor of resistance ' R '. Derive the expression for the instantaneous voltage and current during discharge. (2+2)+6
5. (a) Let a voltage source $V = V_m \sin(\omega t)$ be applied to a RLC circuit connected in series and the corresponding current through the circuit be $I = I_m \sin(\omega t + \phi)$. Find an expression for the total impedance of the circuit and derive the condition for resonance.
 (b) Define bandwidth and half power frequency for the series resonant RLC circuit. (4+3)+3

Unit - II

6. (a) Briefly differentiate among insulators, conductors and semi-conductors.
 (b) Briefly explain drift and diffusion current in connection with a semiconductor.
 (c) Draw the energy band diagram of a P-N junction under reverse bias condition. 3+4+3
7. (a) Draw a neat and labelled diagram of an N-channel JFET, clearly indicating the source, drain and gate terminals.
 (b) Briefly describe the phenomenon of pinch-off in connection to JFET.
 (c) Is JFET a unipolar device or a bipolar device? State the reasons. 4+3+(1+2)
8. (a) Briefly compare a BJT and a FET.
 (b) Describe the construction and basic operation of a depletion type MOSFET.
 (c) Define 'transconductance'. 3+(3+3)+1

Group - B

Answer *question no. 9* and *any four* from the rest, taking *two* from each of **Unit-I** and **Unit-II**.

9. Answer *any five* questions :

2×5

- (a) Define line regulation and load regulation.
- (b) What is the reason for conduction in a Zener diode under reverse-bias condition?
- (c) Define ripple-factor and percentage regulation.
- (d) Define Quiescent point in a transistor.
- (e) What are the factors that affect the stability of an operating point?
- (f) Draw the equivalent circuit of an Op-Amp.
- (g) Define input offset voltage.
- (h) Briefly describe virtual short in connection with Op-Amp.

Unit - I

10. (a) Briefly explain the operation of a bridge rectifier with a neat circuit diagram and timing diagram.
(b) What is a π -type filter? Is it better than a capacitor filter? Explain. 7+(1+1+1)
11. (a) Define the different h-parameters.
(b) Using the h-parameter equivalent circuit of a transistor amplifier connected in CE mode, calculate the following :
(i) Current gain (ii) Voltage gain (iii) Output impedance. 4+6
12. (a) Define the following modes of operation of an amplifier :
(i) Class A (ii) Class AB (iii) Class C.
(b) Briefly describe class B push-pull arrangement of an amplifier. 6+4
13. (a) Explain with neat diagrams, the four types of negative feedback in amplifiers.
(b) Briefly state the advantages and disadvantages of negative feedback. 7+3

Unit - II

14. (a) Briefly explain the concept of virtual ground.
(b) Draw the frequency response of an Op-Amp.
(c) Briefly explain the working of—
(i) Summing amplifier (ii) Inverting amplifier. 3+2+(3+2)

Please Turn Over

- 15.** (a) What is slew rate?
(b) Briefly explain the operation of an integrator.
(c) Draw the circuit diagram of a differential amplifier and explain its operation. 2+4+(1+3)
- 16.** (a) What do you mean by an active filter?
(b) Briefly explain the operation of a high-pass filter constructed using an Op-Amp.
(c) Define cut-off frequency and draw the gain vs frequency curve of an ideal low-pass filter. 2+4+(2+2)
-