T(II)-Electronics-G-2

2021

ELECTRONICS — GENERAL

Second Paper

Full Marks : 100

The figures in the margin indicate full marks. Candidates are required to give their answers in their own words as far as practicable.

Group - A

Answer question no. 1 and any four questions, taking two from each of Unit-I and Unit-II.

1. Answer any five questions :

- (a) What are positive and negative logic systems?
- (b) What is the binary equivalent of $(135.15)_{\circ}$?
- (c) Verify the Boolean identity: A(A+B) = A
- (d) What is the meaning of the term 'Fan-out' with reference to IC gates?
- (e) How can you convert a voltmeter to an ammeter?
- (f) Name two AC Bridges used to measure capacitance.
- (g) What is dual beam CRO?
- (h) What type of DVM has the fastest conversion time?

Unit - I

- 2. (a) Find the dual of the function F = (A'B + AB')
 - (b) Why EX-OR gate is called controlled inverter?

(c) Prove that NAND and NOR gates are universal gates. 2+2+(3+3)

- 3. (a) Design a full adder circuit using NAND gates only.
 - (b) Design a (2×4) decoder using basic gates only.
 - (c) Design a (4×16) decoder using two (3×8) decoders.
- 4. (a) Distinguish decoder and demultiplexer.
 - (b) Design a 8 : 1 multiplexer circuit using two 4 : 1 multiplexer and one 2 : 1 multiplexer.
 - (c) What are the advantages of JK flip flop over SR flip flop?
 - (d) Draw the circuit diagram of a MOD-8 ripple counter.

Please Turn Over

 2×5

2+3+2+3

- 3+3+4

T(II)-Electronics-G-2

- 5. (a) Design an AND gate using discrete circuit components and explain its working principle.
 - (b) Define propagation delay of a logic gate.
 - (c) What are the advantages of CMOS over TTL?
 - (d) What is the minimum number of flip flops required to design a MOD-128 ripple counter?

4+2+2+2

Unit - II

- 6. (a) Draw the block diagram of a general purpose CRO and indicate its basic components.
 - (b) How frequency of an AC signal can be measured using CRO?
 - (c) What is the need for applying a saw-tooth voltage in a CRO? 4+3+3
- 7. (a) What is meant by regulated power supply?
 - (b) Draw the circuit diagram of a fixed +5V regulated power supply using a suitable IC regulator.
 - (c) Explain the operation of a basic DC ammeter. 2+3+5
- 8. (a) Explain with a diagram the operation of a dual-slope digital voltmeter.
 - (b) Draw the circuit and explain the operation of a square wave generator. 5+5

Group-B

Answer question no. 9 and any four questions, taking two from each of Unit-I and Unit-II.

- 9. Answer *any five* questions :
 - (a) What is dielectric polarization?
 - (b) Write down the relation between electric field and electric potential.
 - (c) What is noise figure?
 - (d) What is signal to noise ratio (SNR)?
 - (e) What is modulation index in FM?
 - (f) What is reflection coefficient of a transmission line?
 - (g) What is PWM?
 - (h) What is Nyquist rate in pulse communication?

Unit - I

- **10.** (a) What is current density?
 - (b) Write down integral and differential forms of Gauss's law in electrostatics.
 - (c) What is equipotential surface? Show by drawing, the nature of the lines of force and equipotential surfaces around a charged spherical ball.
 2+(2+2)+(2+2)

 2×5

2+6+2

- 11. (a) State Faraday's laws of electromagnetic induction.
 - (b) What is Lorentz force?
 - (c) Compare ferromagnetic, paramagnetic and diamagnetic materials.
 - (d) Calculate the flux density at a distance of 1 cm from a long straight wire carrying a current of 25A and placed in air. 2+2+3+3
- 12. (a) What is meant by 'characteristic impedance' of a transmission line?
 - (b) Derive transmission line equations in terms of voltage and current.
 - (c) What is a coaxial cable?
- 13. (a) What are the different types of transmission line used?
 - (b) Derive the relation between line impedance and reflection coefficient of a loss-less transmission line.
 - (c) Explain the primary and secondary constants of a transmission line. 2+5+3

Unit-II

- 14. (a) What is meant by TE and TM modes in a waveguide?
 - (b) What is the cut off wavelength of a waveguide?
 - (c) Write the relation between the guide-wavelength, cut-off wavelength and the free-space wavelength in a waveguide.
 - (d) Define phase velocity and group velocity in a waveguide.
 - (e) What is the difference between a transmission line and a waveguide? 2+2+2+2+2
- **15.** (a) Why is modulation needed?
 - (b) Obtain an expression for an AM wave with sinusoidal modulation. Draw the message signal, carrier signal and AM waveforms.
 - (c) What is depth of modulation? 2+(3+3)+2

16. (a) Compare AM and FM.

- (b) Derive the relation between total power and carrier power of a 100% modulated AM wave.
- (c) Why is sky wave reception better during night time?
- (d) What is skip distance?

2+4+2+2